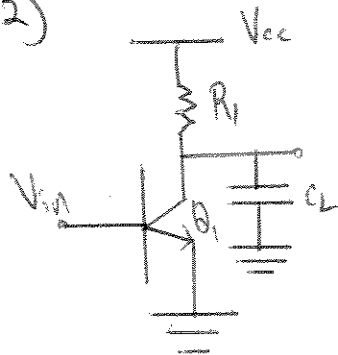


2)



-3dB bandwidth = 1 GHz

$C_L = 2 \text{ pF}$

Power = 2 mW

Low freq gain?

$$\text{Power} = 2.5V I_c, \quad I_c = 0.8 \text{ mA}$$


$$\text{Dominant Pole at the output} = \frac{1}{R_L C_L} = 2\pi (1 \text{ GHz})$$

$$R_L = 79.58 \text{ Ohm}$$


$$\text{Low Freq gain: } -g_m R_L = \frac{-I_c R_L}{V_T} = \frac{(79.58)(0.8)}{26}$$

$$A_v \Big|_{\text{low freq}} = -2.45$$


4)

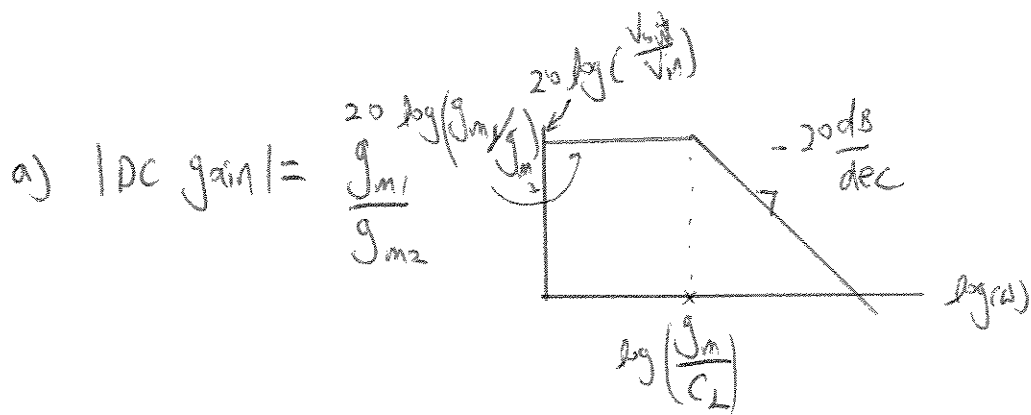


b)  $|DC \text{ gain}| = g_{m1} \left( \frac{1}{g_{m2}} + \frac{R_B}{\beta + 1} \right)$

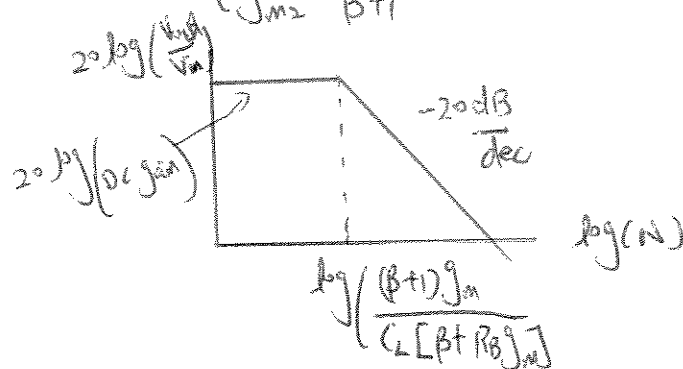


c)  $|DC \text{ gain}| = g_{m1} (V_{o1}/V_{o2})$

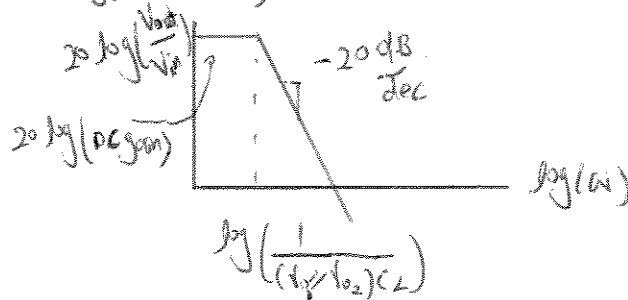

d)  $|DC \text{ gain}| = g_{m1}/g_{m2}$

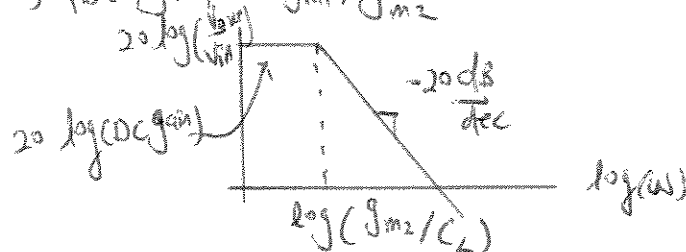

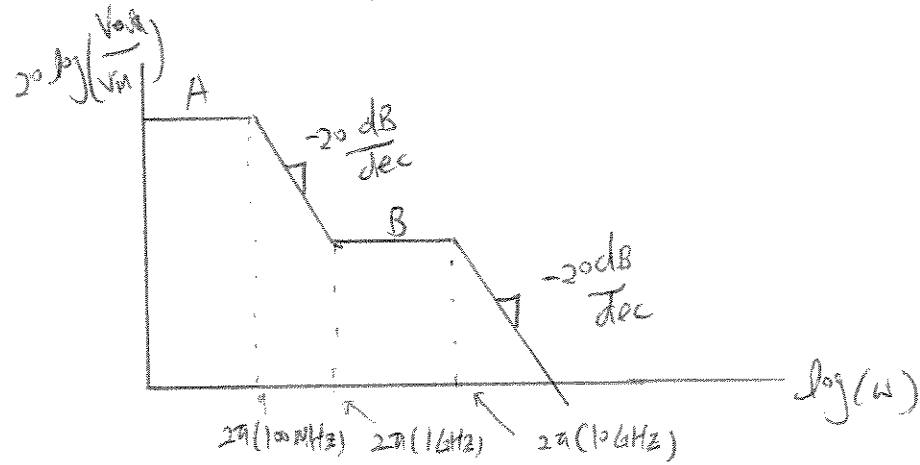
6)  
 Poles at 100 MHz, 10 GHz  
 Zero at 1 GHz.




$$A(100 \text{ MHz}) = B(1 \text{ GHz})$$

$$B = 0.1A$$

8) Ideal differentiator:  $S = \frac{V_{out}}{V_{in}}$ ,  $\left| \frac{V_{out}}{V_{in}}(j\omega) \right| = \omega$   
 $\omega_z = 0$

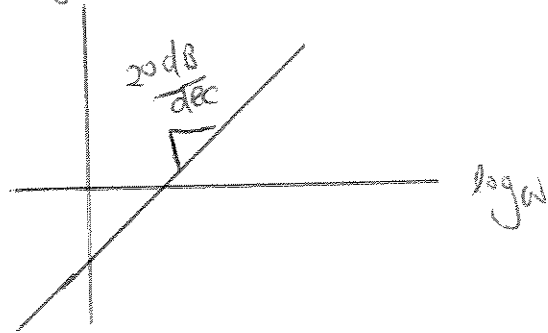

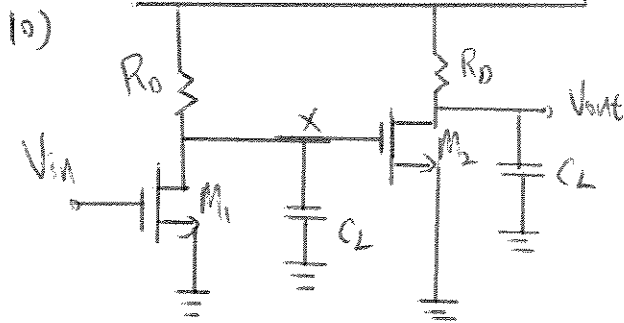For an ideal differentiator, gain at arbitrary high freq approaches infinity.



$$\frac{V_x(s)}{V_{in}} = -g_m \left( R_D \parallel \frac{1}{C_L s} \right), \quad \frac{V_{out}(s)}{V_x} = -g_m \left( \frac{R_D}{R_D C_L s + 1} \right)$$

$$= -g_m \left( \frac{R_D}{R_D C_L s + 1} \right)$$

$$H(s) = \frac{V_x(s)}{V_{in}} \frac{V_{out}(s)}{V_x} = \left( \frac{g_m R_D}{R_D C_L s + 1} \right)^2$$

$$s \rightarrow j\omega, \quad H(j\omega) = \left( \frac{g_m R_D}{1 + R_D C_L j\omega} \right)^2$$

$$|H(j\omega)| = \frac{(g_m R_D)^2}{1 + (R_D C_L \omega)^2}$$

-3dB Bandwidth:


$$\frac{(g_m R_D)^2}{1 + (R_D C_L \omega)^2} = \frac{(g_m R_D)^2}{\sqrt{2}}$$

$$\Rightarrow (R_D C_L \omega)^2 + 1 = \sqrt{2}$$

$$\Rightarrow \omega = \frac{\sqrt{\sqrt{2}-1}}{R_D C_L} = \frac{0.6436}{R_D C_L} \left( \frac{\text{rad}}{\text{s}} \right)$$

$$2\pi f = \frac{0.6436}{R_D C_L} \Rightarrow f = \frac{0.10243}{R_D C_L} \text{ (Hz)}$$

12)

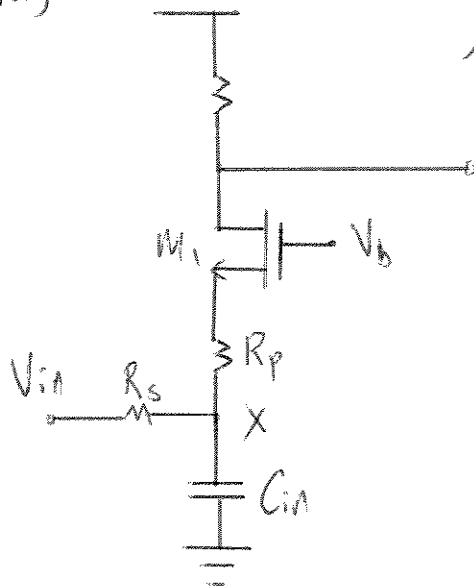


To find input pole,  
let  $V_{in} = 0$  and  
find the equivalent  
resistance and capacitance  
from node X to  
ground.

$$R_x = R_s \parallel \left( R_p + \frac{1}{g_{m_1}} \right), \quad C_x = C_{in}$$

$$\omega_{p.in} = \frac{1}{C_{in} \left[ R_s \parallel \left( R_p + \frac{1}{g_m} \right) \right]}$$

$$\omega_{p.out} = \frac{1}{R_o C_L}$$

14)

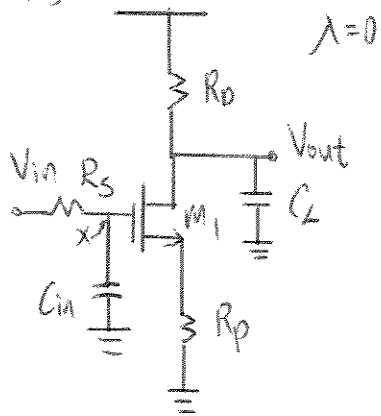


$$R_x = R_s, \quad R_{out} = R_D$$

$$C_x = C_{in}, \quad C_{out} = C_L$$

$$\omega_{pin} = \frac{1}{R_s C_{in}}, \quad \omega_{pout} = \frac{1}{R_D C_L}$$


16)

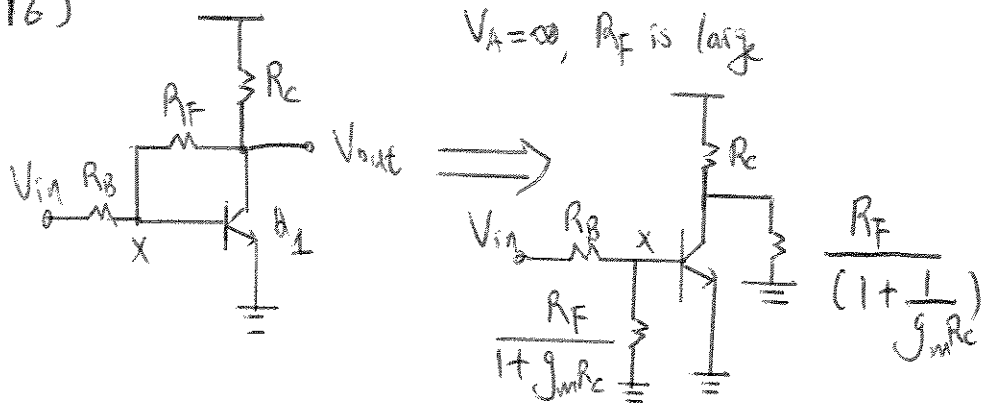

$$R_x = R_B \parallel \left( \frac{R_F}{1 + g_m R_C} \right), \quad R_{out} = R_C \parallel \left( \frac{R_F}{1 + \frac{1}{g_m R_C}} \right)$$
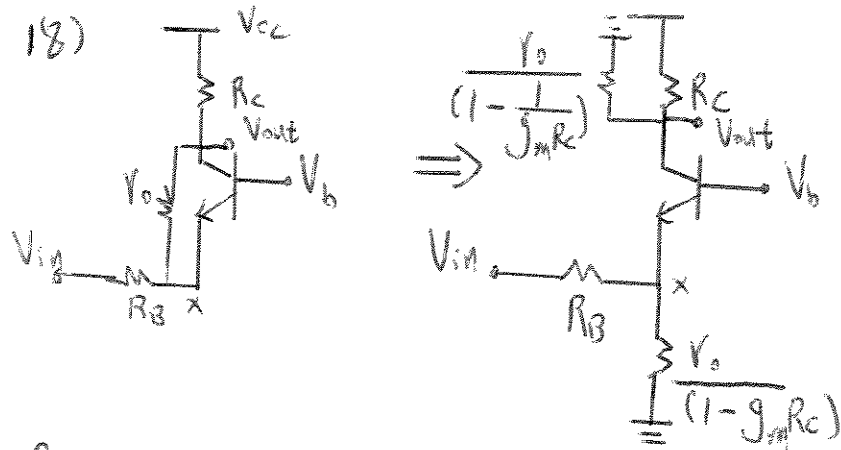
$$\frac{V_{out}}{V_{in}} = \frac{-R_{out}}{\frac{1}{g_m} + \frac{R_x}{\beta + 1}} = \frac{-R_C \parallel \left( \frac{R_F}{1 + 1/g_m R_C} \right)}{\frac{1}{g_m} + \frac{R_B \parallel (R_F / (1 + g_m R_C))}{\beta + 1}}$$






$$R_{out} = R_C \parallel \left( \frac{V_o}{1 - \frac{1}{g_m R_C}} \right)$$

$$R_x = R_B \parallel \left( \frac{V_o}{1 - g_m R_C} \right)$$

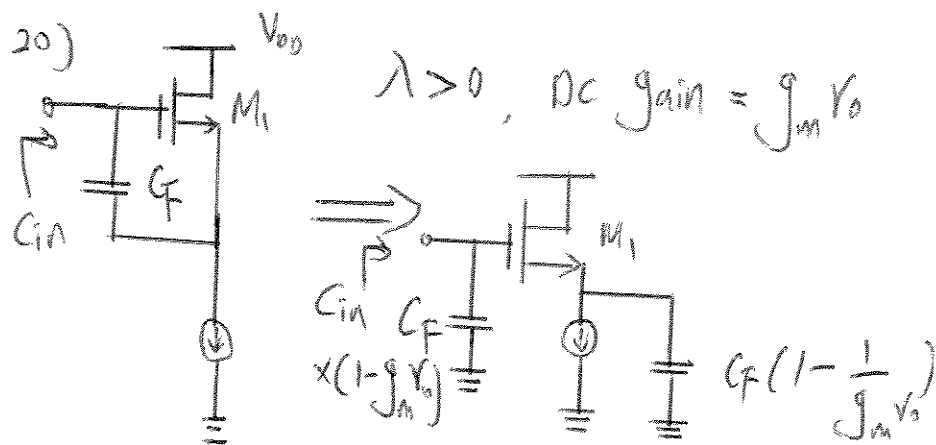
$$\frac{V_{out}}{V_{in}} = \frac{R_{out}}{R_x + \frac{1}{g_m}} = \frac{R_C \parallel \left( \frac{V_o}{1 - \frac{1}{g_m R_C}} \right)}{R_B \parallel \left( \frac{V_o}{1 - g_m R_C} \right) + \frac{1}{g_m}}$$




$$C_{in} = C_f (1 - g_m r_o)$$

As  $\lambda \rightarrow 0$ ,  $r_o \rightarrow \infty$ ,  $g_m r_o \rightarrow \infty$ ,  $C_{in} = -\infty$

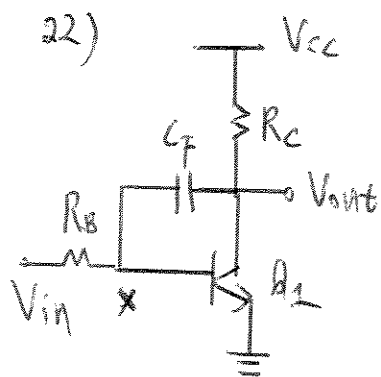When  $C \rightarrow$  negative in value, we have inductive activity. So right here, we have an effective infinite inductor.



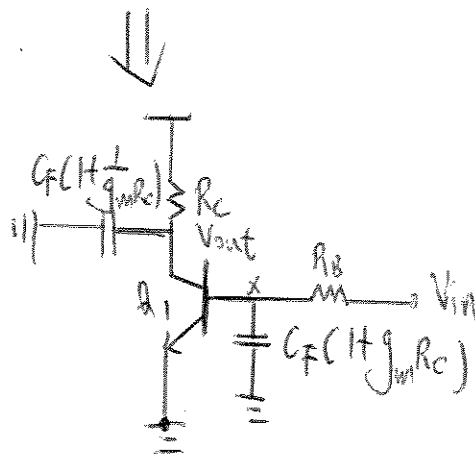DC gain (from  $x$  to out):  
 $-g_m R_c$



$$C_{in} = C_F (1 + g_m R_c)$$

$$R_{in} = R_B \parallel Y_{\pi}$$


$$C_{out} = C_F (1 + \frac{1}{g_m R_c})$$

$$R_{out} = R_c$$

$$\omega_{p1} = \frac{1}{R_B \parallel Y_{\pi} [C_F (1 + g_m R_c)]}$$

$$\omega_{pout} = \frac{1}{R_c C_F (1 + \frac{1}{g_m R_c})} \approx \frac{1}{R_c C_F}$$


$$(\text{if } g_m R_c \gg 1)$$

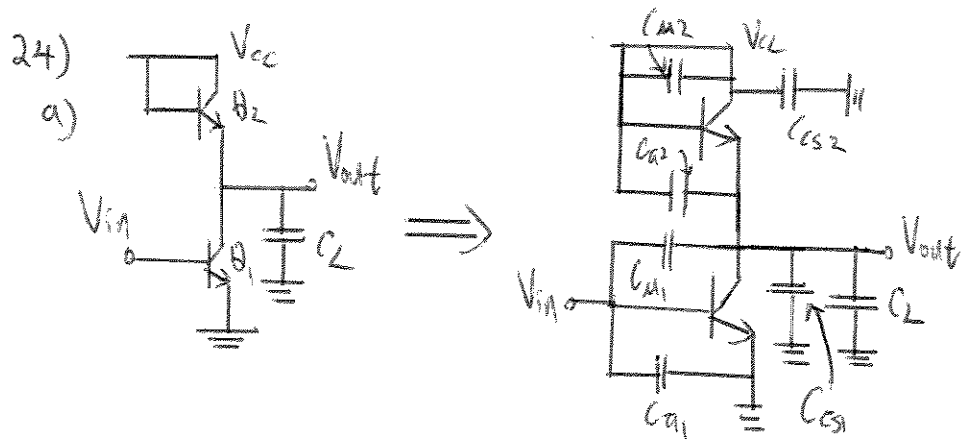

$C_{M2}, C_{cs1}, C_L$  are in parallel

$C_{M2}, C_{cs2}$  are grounded on both ends.

(and technically in parallel as well)


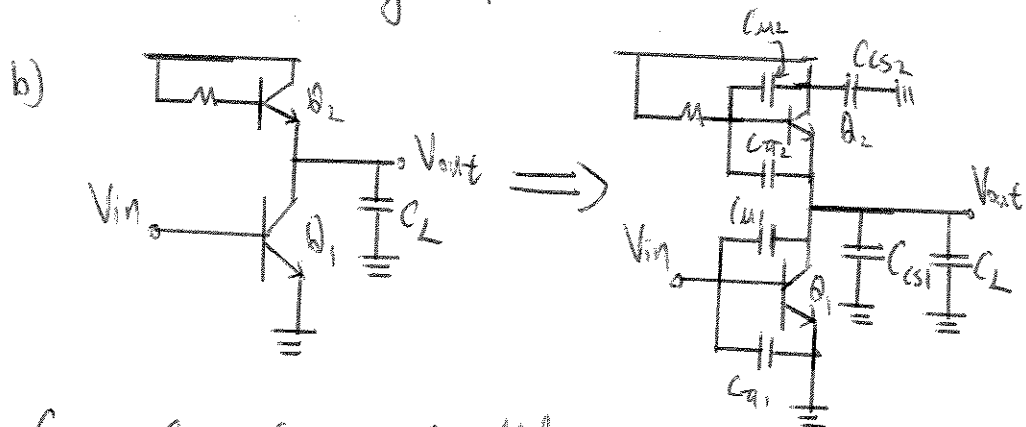


$C_{cs1}, C_L$  are in parallel

$C_{cs2}$  is grounded on both ends

24)

c)

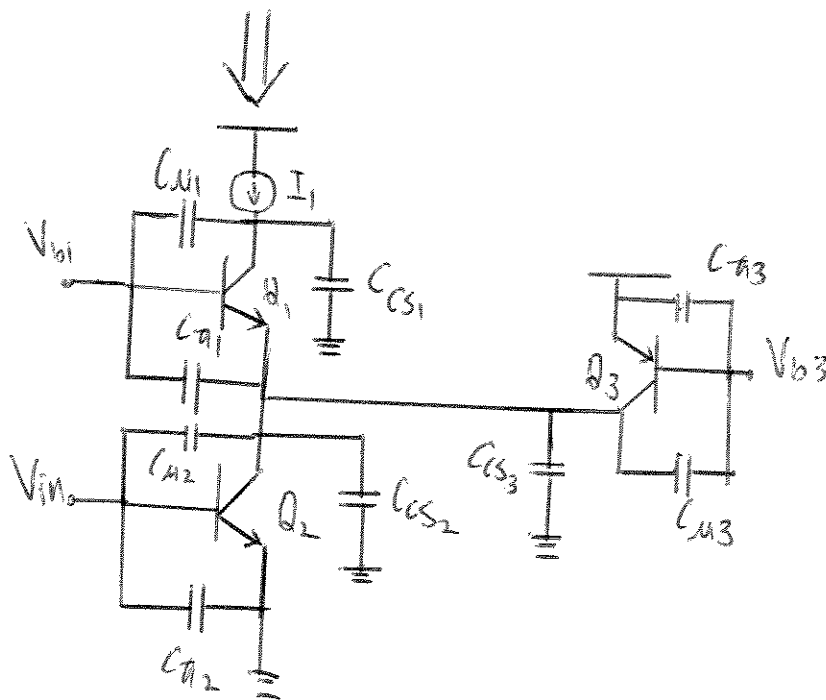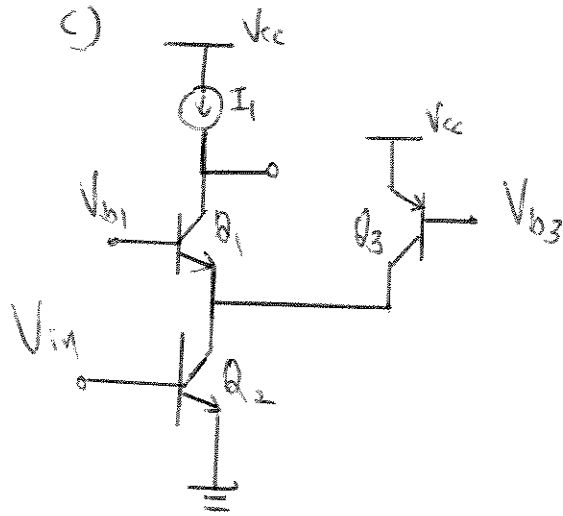


$C_{\pi 1}$ ,  $C_{CS2}$ ,  $C_{CS3}$ ,  $C_{\mu 3}$  are in parallel  
 $C_{\mu 1}$ ,  $C_{CS1}$  are also in parallel

$C_{\pi 3}$  is grounded on both ends

26)

Bipolar

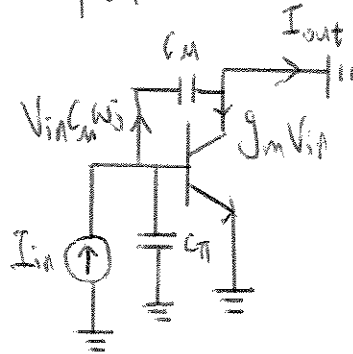


$$V_{in} = (I_{in}) \left( \frac{1}{[C_M + C_\pi] \omega j} \right) \quad (\text{Assuming we are at freq, and } V_A \text{ can be neglected})$$

$$I_{out} = V_{in} C_M \omega j - g_m I_{in} \left( \frac{1}{[C_M + C_\pi] \omega j} \right)$$

$$\frac{I_{out}}{I_{in}} = \frac{C_M \omega j - g_m}{[C_M + C_\pi] \omega j} \Rightarrow \left| \frac{I_{out}}{I_{in}} \right| = \frac{\sqrt{(g_m)^2 + (C_M \omega)^2}}{[C_M + C_\pi] \omega} = 1$$
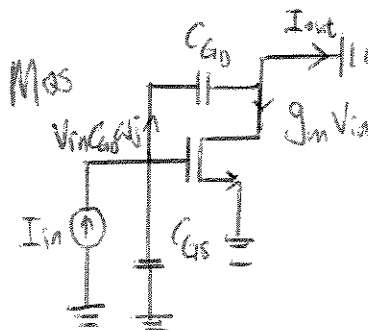
$$\omega_T^2 = \frac{g_m^2}{2 C_M C_\pi + C_\pi^2} \Rightarrow \omega_T = 2\pi f_T = \frac{g_m}{\sqrt{2 C_M C_\pi + C_\pi^2}}$$



Similarly for MOS, with  $C_M$  and  $C_\pi$  replaced by  $C_{gd}$  and  $C_{gs}$  respectively.

$$\omega_T = 2\pi f_T = \frac{g_m}{\sqrt{2 C_{gd} C_{gs} + C_{gs}^2}}$$

28)

$$C_{gs} \approx \left(\frac{2}{3}\right) WL C_{ox}$$

$$2\pi f_T = \frac{g_m}{C_{gs}} = \frac{\frac{W}{L} \mu_n C_{ox} (V_{GS} - V_{TH})}{\frac{2}{3} WL C_{ox}}$$


$$2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$$

30)

a) As  $W \uparrow$ ,  $(V_{GS} - V_{TH})$  has to  $\downarrow$  by

$\frac{1}{\sqrt{W}}$  in order to maintain  $I_0$  constant  
 using equation  $2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$


$$2\pi f_T \propto \frac{1}{\sqrt{W}}$$

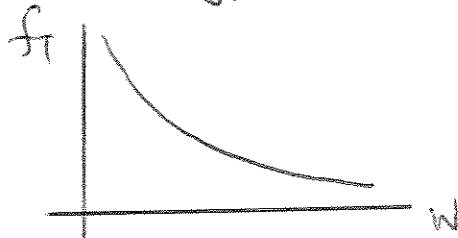

b)  $I_0 \uparrow$ ,  $W$  constant it means  $V_{GS} - V_{TH} \uparrow$

With  $\sqrt{I_0}$ . Using equation  $2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$

$$2\pi f_T \propto \sqrt{I_0}$$

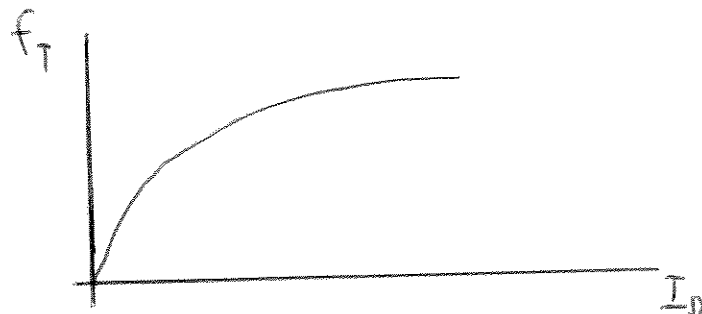




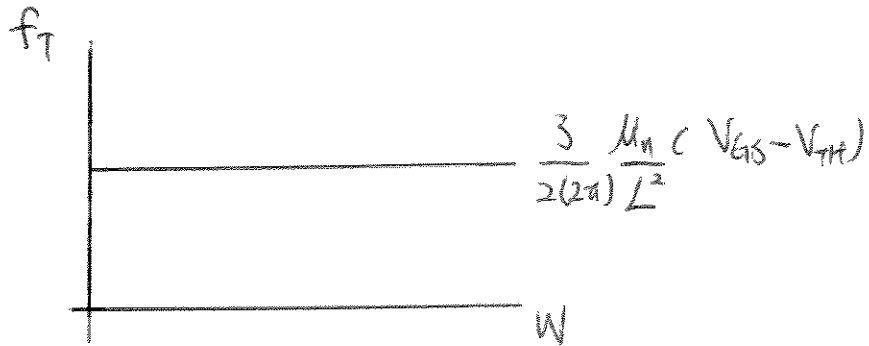32) a)


Using equation  $2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$

We know that  $2\pi f_T$  is constant for all  $W$ .



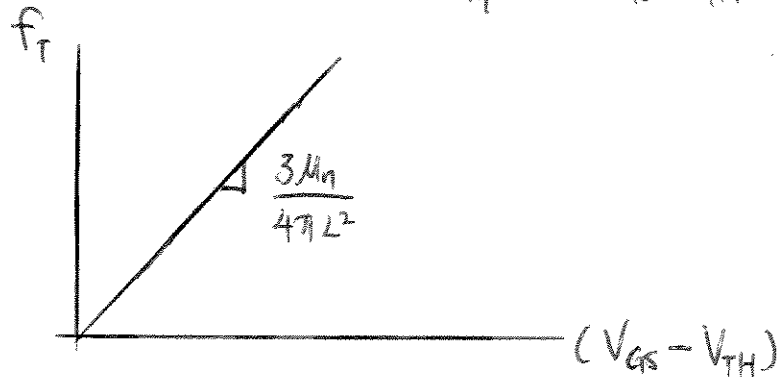b) Using equation  $2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$ ,

We know that  $2\pi f_T \propto (V_{GS} - V_{TH})$ .



34)

$$a) V_{GS} - V_{TH} \rightarrow \frac{1}{2} (V_{GS} - V_{TH})$$

Constant  $I_D$  and  $W \uparrow$  ( $L$  constant)

$$2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$$

$$f_{T_{\text{new}}} = \frac{f_{T, \text{old}}}{2}$$


$$b) V_{GS} - V_{TH} \rightarrow \frac{1}{2} (V_{GS} - V_{TH})$$

Constant  $W$  and  $I_D \downarrow$  ( $L$  constant)

$$2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$$

$$f_{T_{\text{new}}} = \frac{f_{T, \text{old}}}{2}$$

36)

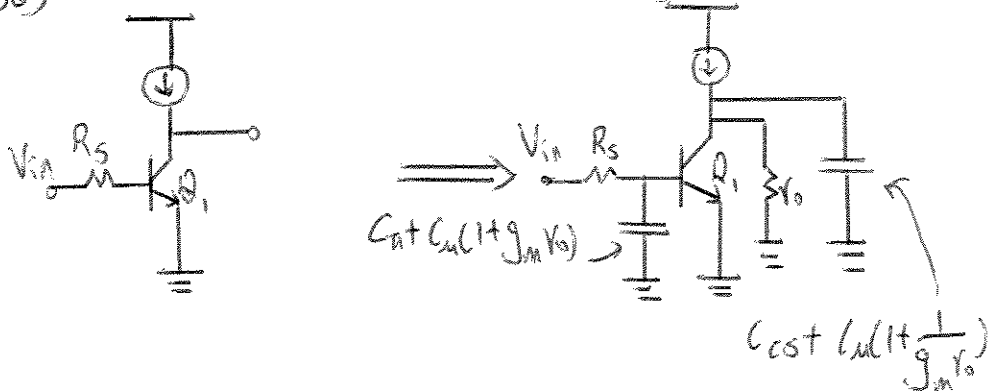

$$\omega_{pin} = \frac{1}{(R_s \parallel r_{\pi}) [C_{\pi} + C_{\mu}(1 + g_m r_o)]}$$


$$\omega_{pout} = \frac{1}{r_o [C_{cs} + C_{\mu}(1 + 1/g_m r_o)]}$$

$$H(s) = \frac{DC \text{ gain}}{\left(1 + \frac{s}{\omega_{pin}}\right) \left(1 + \frac{s}{\omega_{pout}}\right)}$$

$$H(s) = \frac{g_m r_o (r_{\pi} / (r_{\pi} + R_s))}{\left(1 + \frac{s}{1 / (R_s \parallel r_{\pi}) [C_{\pi} + C_{\mu}(1 + g_m r_o)]}\right) \left(1 + \frac{s}{1 / (r_o [C_{cs} + C_{\mu}(1 + 1/g_m r_o)])}\right)}$$


38)

a)

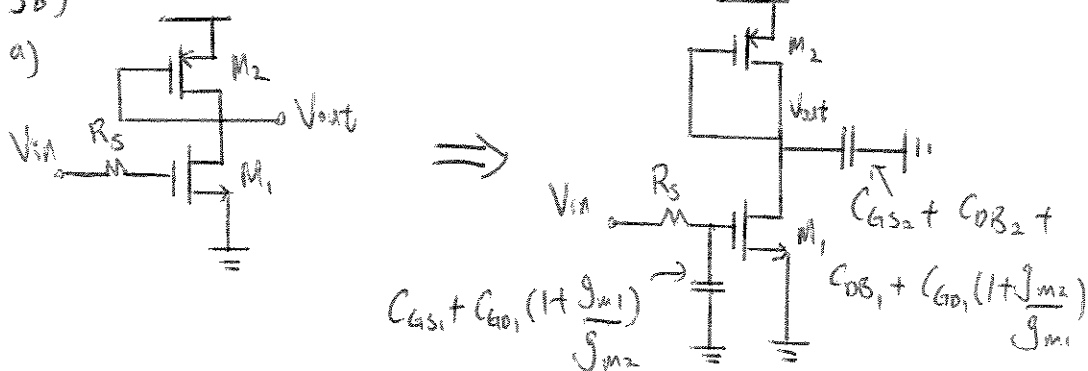

$$DC \text{ gain} = -g_{m1} (r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}}) \approx -\frac{g_{m1}}{g_{m2}}$$
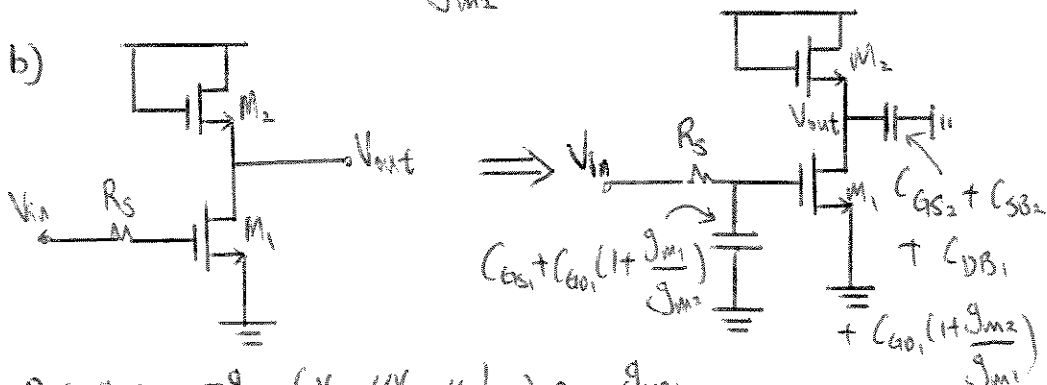
$$\omega_{pin} = \frac{1}{R_s (C_{GS1} + C_{GD1} (1 + \frac{g_{m1}}{g_{m2}}))} \quad \omega_{pout} = \frac{g_{m2}}{(C_{GS2} + C_{DB2} + C_{DB1} + C_{GD1} (1 + \frac{g_{m2}}{g_{m1}}))}$$




$$DC \text{ gain} = -g_{m1} (r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}}) \approx -\frac{g_{m1}}{g_{m2}}$$

$$\omega_{pin} = \frac{1}{R_s (C_{GS1} + C_{GD1} (1 + \frac{g_{m1}}{g_{m2}}))}$$

$$\omega_{pout} = \frac{g_{m2}}{C_{SB2} + C_{GS2} + C_{DB1} + C_{GD1} (1 + \frac{g_{m2}}{g_{m1}})}$$

38)

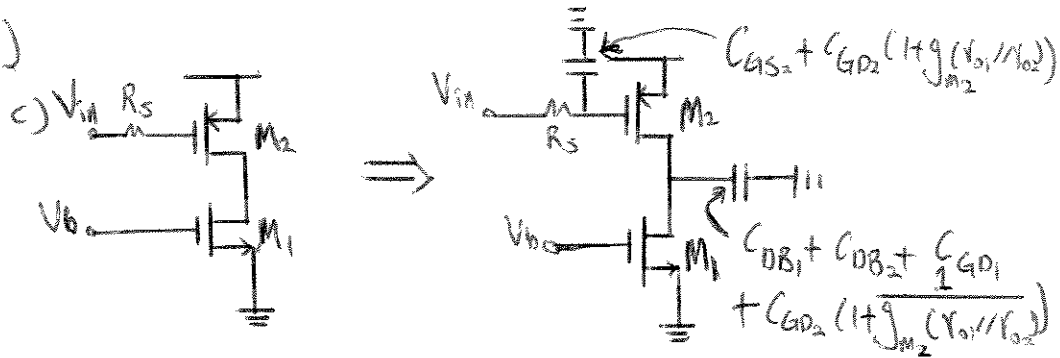

DC gain:  $-g_{m2} (V_{o1} // V_{o2})$


$$\omega_{pin} = \frac{1}{R_s (C_{gs2} + C_{gd2} (1 + g_{m2} (V_{o1} // V_{o2})))}$$

$$\omega_{pout} = \frac{1}{(V_{o1} // V_{o2}) [C_{db1} + C_{db2} + C_{gd1} + C_{gd2} (1 + \frac{1}{g_{m2} (V_{o1} // V_{o2})})]}$$


$$\omega_{pout} \approx \frac{1}{(V_{o1} // V_{o2}) [C_{db1} + C_{db2} + C_{gd1} + C_{gd2}]}$$

Since  $g_{m2} (V_{o1} // V_{o2}) \gg 1$

40)

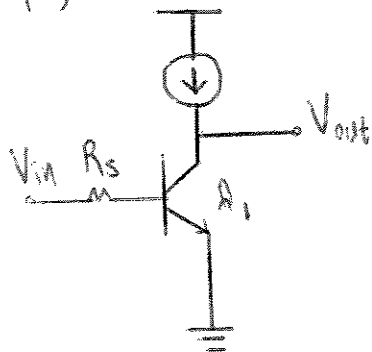

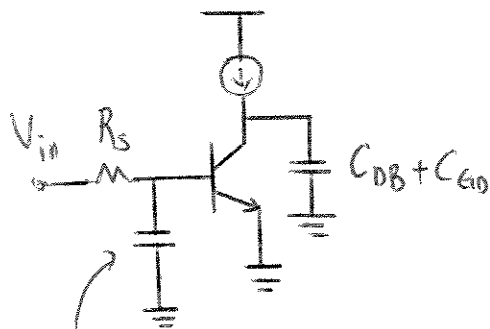a) Miller's Approximation: DC gain:  $-\infty$



$C_{GS} + \infty$

$$\omega_{pin} = \frac{1}{R_S(\infty)} = 0, \quad \omega_{part} = \frac{1}{\infty(C_{DB} + C_{GD})} = 0$$

b) Transfer Function:

$$\frac{V_{out}}{V_{thev}}(s) = \frac{(C_{xy}s - g_m)R_L}{as^2 + bs + 1}$$

$$a = R_{Thev}R_L(C_{in}C_{xy} + C_{out}C_{xy} + C_{in}C_{out})$$

$$b = (1 + g_mR_L)C_{xy}R_{Thev} + R_{Thev}C_{in} + R_L(C_{xy} + C_{out})$$

40)

b)  $R_L \rightarrow \infty$

$$\frac{V_{out}}{V_{thv}} = \frac{C_{xy} S - g_m}{S [R_{thv} (C_{in} C_{xy} + C_{out} C_{xy} + C_{in} C_{out}) S + g_m C_{xy} R_{thv} + (C_{xy} + C_{out})]}$$

So  $\omega_{p1} = 0$

$$\omega_{p2} = \frac{(g_m C_{xy} R_{thv} + (C_{xy} + C_{out}))}{R_{thv} [C_{in} C_{xy} + C_{out} C_{xy} + C_{in} C_{out}]}$$

$$\omega_{p2} = \frac{g_m C_u R_S / R_n + C_u + C_{cs}}{R_S / R_n [C_n C_u + C_{cs} C_u + C_n C_{cs}]}$$

$\omega_{p1} = \omega_{pin}, \quad \omega_{p2} = \omega_{pout}.$


Miller:

$\omega_{pin} = 0, \quad \omega_{pout} = 0$

Again, the output pole predicted by the transfer function is pushed out, and the input poles are similar. (In fact, they are the same this time.)

This shows one of the short-comings of Miller's approximation.

42)

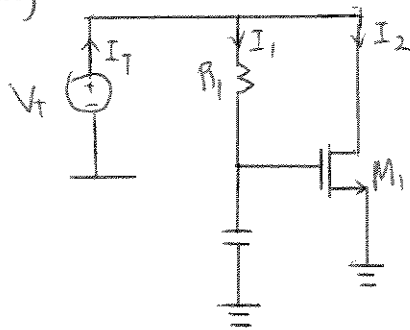

$\lambda=0$ , and neglect other capacitances.

$$I_T = I_1 + I_2$$

$$I_1 = \frac{V_T}{(R_1 + \frac{1}{C_1 s})}, \quad I_2 = \frac{g_{m1} V_T}{C_1 R_1 s + 1}$$


$$I_T = \frac{C_1 s V_T}{C_1 R_1 s + 1} + \frac{g_{m1} V_T}{C_1 R_1 s + 1} \Rightarrow \frac{V_T}{I_T} = \frac{C_1 R_1 s + 1}{C_1 s + g_{m1}}$$

$$s \rightarrow j\omega \Rightarrow \frac{C_1 R_1 (j\omega) + 1}{C_1 j\omega + g_{m1}} = Z_T(j\omega)$$

$$|Z_T| = |Z_{in}| = \frac{\sqrt{(C_1 R_1 \omega)^2 + 1}}{\sqrt{C_1^2 \omega^2 + g_{m1}^2}} = \frac{\sqrt{C_1 R_1 \omega^2 + 1}}{g_{m1} \sqrt{\left(\frac{C_1 \omega}{g_{m1}}\right)^2 + 1}}$$

At  $\omega = \frac{1}{C_1 R_1}$ , we have a zero, at  $\omega = \frac{g_{m1}}{C_1}$ , we have a pole. If  $R_1 > \frac{1}{g_{m1}}$ , the zero  $\frac{1}{C_1 R_1}$  is at a lower frequency than the pole, and the bode-plot for magnitude would look like the following.


$20 \log(Z_{in})$

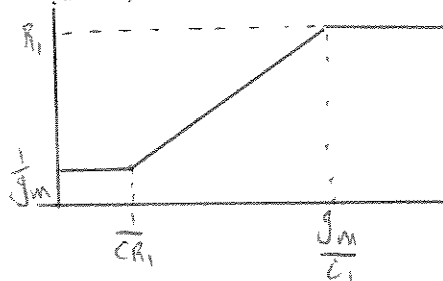

The bode-plot shows an impedance that increases with frequency, an inductive behavior.



44)

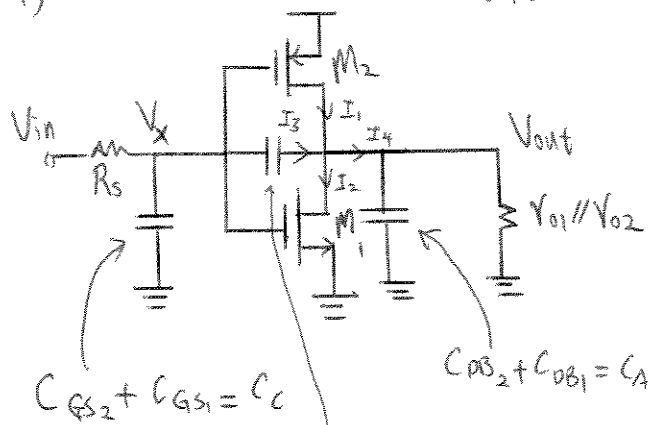 $\lambda > 0$ 

$$V_{out} = I_4 (Y_{01} // Y_{02} // \frac{1}{[C_{db2} + C_{db1}]s}) \quad \xrightarrow{Z_{out}}$$

$$I_4 = I_1 + I_3 - I_2$$

$$I_1 = (0 - V_x) g_{m2}$$

$$I_2 = V_x g_{m1}$$

$$I_3 = (V_x - V_{out}) (C_{gd1} + C_{gd2}) s$$

$$I_4 = -V_x g_{m2} + (V_x - V_{out}) C_B s - V_x g_{m1}$$

$$V_{out} = Z_{out} [-V_x (g_{m2} + g_{m1}) + (V_x - V_{out}) C_B s]$$

Writing a node equation at X.

$$\frac{V_x - V_{in}}{R_s} + V_x C_c s + (V_x - V_{out}) C_B s = 0$$

$$V_x = \frac{V_{out} C_B s + V_{in}/R_s}{(1/R_s + C_c s + C_B s)}$$

44)

Substitute everything and we get

$$V_{out} = Z_{out} \left[ -(g_{m1} + g_{m2}) \left( \frac{V_{out} C_B s + V_{in}/R_s}{1/R_s + C_c s + C_B s} \right) + \left( \frac{V_{out} C_B s + V_{in}/R_s}{1/R_s + C_c s + C_B s} - V_{out} \right) C_B s \right]$$

Collect all the  $V_{out}$ 's on one-side and likewise for  $V_{in}$ 's,  
we will get

$$\frac{V_{out}}{V_{in}} = \frac{Z_{out} (C_B s - (g_{m1} + g_{m2}))}{\frac{1}{R_s} + (C_c + C_B) s + Z_{out} C_B s (g_{m1} + g_{m2}) + Z_{out} C_B s \left( \frac{1}{R_s} + (C_c + C_B) s \right) - Z_{out} C_B^2 s^2}$$


$$\text{where } Z_{out} = Y_{o1} // Y_{o2} // \frac{1}{[C_{DB1} + C_{DB2}] s}$$

$$C_B = C_{GD1} + C_{GD2}$$

$$C_c = C_{GS1} + C_{GS2}$$

46)

a)

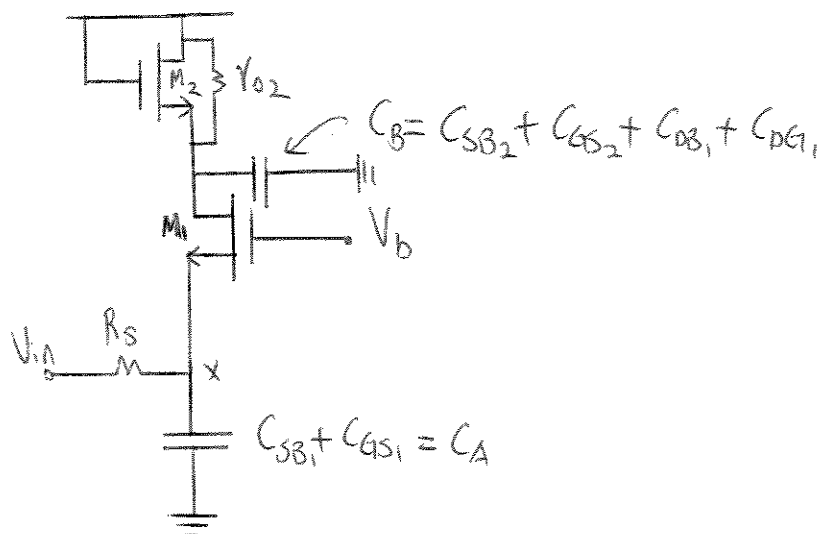

$$V_{out} = -(0 - V_x) g_{m1} \left[ \frac{1}{g_{m2}} \parallel \frac{1}{C_B s} \right] = V_x g_{m1} \left[ \frac{1}{g_{m2}} \parallel \frac{1}{C_B s} \right]$$

Node equation at X,  $\frac{V_x - V_{in}}{R_s} + V_x C_A s - g_m (0 - V_x) = 0$

$$V_x \left( \frac{1}{R_s} + C_A s + g_m \right) = \frac{V_{in}}{R_s} \Rightarrow V_x = \frac{V_{in}}{(1 + R_s C_A s + R_s g_m)}$$

substitute in  $V_x$  and solving for  $V_{out}/V_{in} \Rightarrow$


$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} \left[ \frac{1}{g_{m2}} \parallel \frac{1}{C_B s} \right]}{(1 + R_s C_A s + R_s g_m)}$$

$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} (1/g_{m2})}{(C_B (1/g_{m2}) s + 1) (1 + R_s C_A s + R_s g_m)}$$

Where  $C_B = C_{sb2} + C_{gs2} + C_{db1} + C_{db2}$

$C_A = C_{sb1} + C_{gs1}$

46)

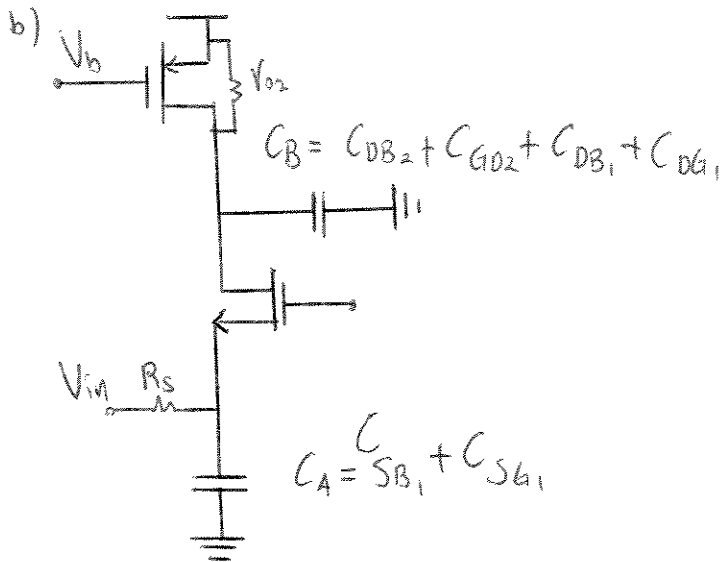

Similar to part a), with  $\frac{1}{g_{m2}}$  replaced by  $V_{o2}$ ,  
and different  $C_B$ .


$$\text{So } \frac{V_{out}}{V_{in}} = \frac{g_{m1} V_{o2}}{(C_B V_o s + 1)(1 + R_s C_A s + R_s g_{m1})}$$

Where  $C_B = C_{DB2} + C_{GD2} + C_{DB1} + C_{DG1}$

$$C_A = C_{SB1} + C_{SG1}$$

46)

c)

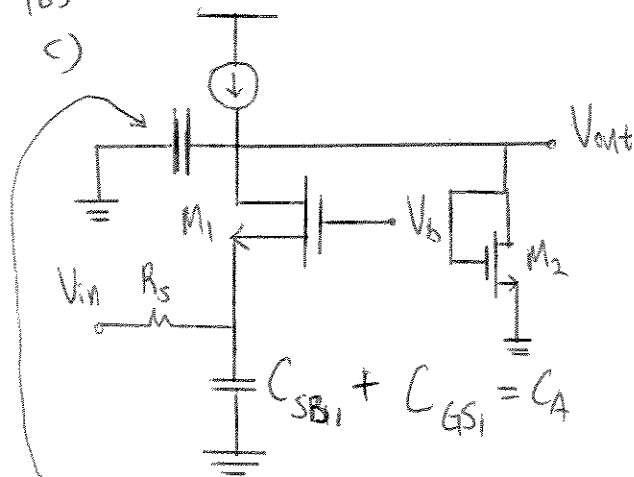

$$C_B = C_{DB1} + C_{GD1} + C_{DB2} + C_{GS2}$$


AC-wise, this circuit is very similar to part a). Its transfer function is the same as part a), except for  $C_B$ .

$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} (1/g_{m2})}{(C_B (1/g_{m2}) s + 1) (1 + R_S C_A s + R_S g_{m1})}$$

Where  $C_B = C_{DB1} + C_{GD1} + C_{DB2} + C_{GS2}$

$$C_A = C_{SB1} + C_{GS1}$$

48)

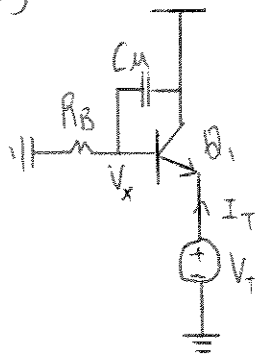

$$V_A = \infty$$

$$\frac{\beta}{\beta+1} \approx 1, \text{ if } \beta \gg 1$$

$$I_T = -(V_x - V_T) g_m \approx -(V_x - V_T) g_m$$

$$V_x = \frac{I_T}{\beta} \left( R_B \parallel \frac{1}{C_u s} \right)$$

$$I_T = \left( V_T - \frac{I_T}{\beta} \left( R_B \parallel \frac{1}{C_u s} \right) \right) g_m$$

$$I_T = g_m V_T - \frac{g_m}{\beta} \left( R_B \parallel \frac{1}{C_u s} \right) I_T$$

$$I_T \left( 1 + \frac{g_m}{\beta} \left( R_B \parallel \frac{1}{C_u s} \right) \right) = g_m V_T$$


$$\frac{V_T}{I_T} = \frac{1}{g_m} + \frac{R_B \parallel \frac{1}{C_u s}}{\beta} = \frac{\beta C_u R_B (s + \frac{\beta + R_B g_m}{\beta C_u R_B})}{g_m \beta (1 + C_u R_B s)}$$

$$\text{Zero: } \frac{\beta + R_B g_m}{\beta C_u R_B}, \quad \text{Pole: } \frac{1}{C_u R_B}$$


$$\text{At DC, } |Z_{out}| = \frac{1}{g_m} + \frac{R_B}{\beta}$$

$$\text{At very high freq: } |Z_{out}| = \frac{1}{g_m}$$

$20 \log |Z_{out}|$

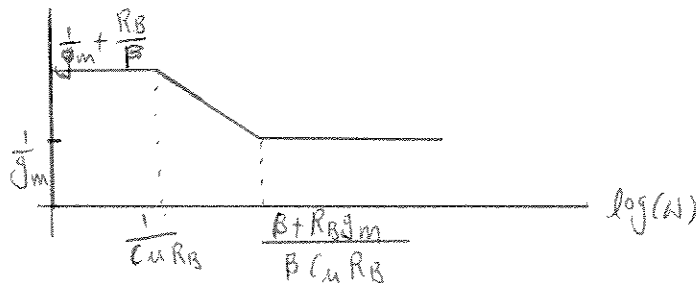

50)

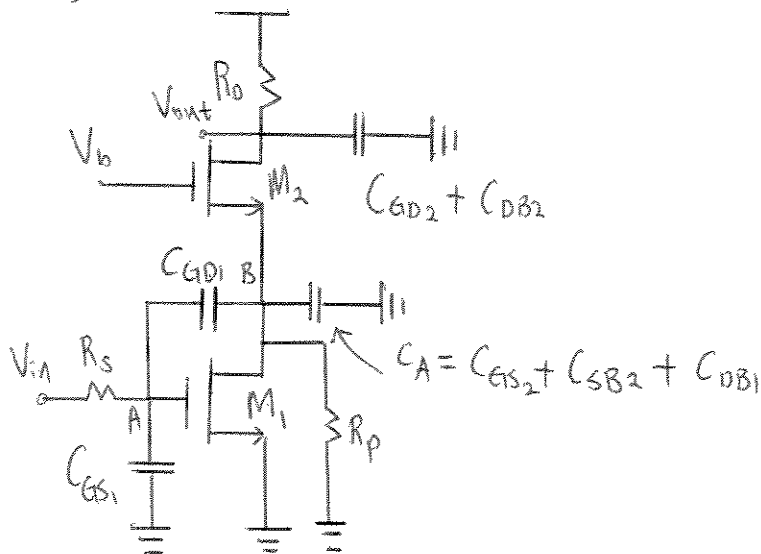

DC gain from A to B is  $-g_{m1}(R_p \parallel \frac{1}{g_{m2}})$


Applying Miller's Theorem:

$$\omega_{pin}(\omega_{pA}) = \frac{1}{R_s(C_{GS1} + C_{GD1}(1 + g_{m1}(R_p \parallel \frac{1}{g_{m2}})) )}$$

$$\omega_{pB} = \frac{1}{R_p \parallel \frac{1}{g_{m2}} [C_{GS2} + C_{DB2} + C_{DB1} + C_{GD1}(1 + 1/g_{m1}(R_p \parallel \frac{1}{g_{m2}}))]}$$

$$\omega_{pout} = \frac{1}{R_o(C_{GD2} + C_{DB2})}$$

52)

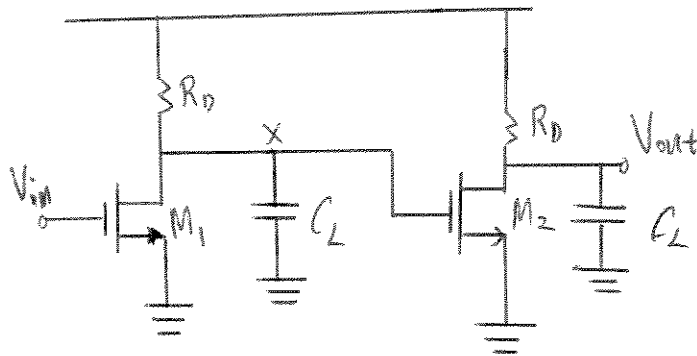

Bias Current = 1mA (each stage)

$$C_L = 50 \text{ fF}$$

$$\mu_n C_{ox} = 100 \mu\text{A/V}^2, A_v = 20, -3\text{dB: } 1\text{GHz}$$

$$\text{DC gain: } (g_m R_D)^2 = 20$$

$$-3\text{dB bandwidth: } 0.10243 / (R_D C_L) = 1\text{GHz}$$

$$\text{Since } C_L = 50 \text{ fF}, R_D = 2048.6 \Omega$$

$$(g_m R_D)^2 = 20 \Rightarrow g_m = 0.002183 = \frac{2I_D}{V_{eff}} \Rightarrow V_{eff} = 0.916\text{V}$$

$$V_{eff} = V_{GS} - V_{th} = 0.916\text{V}$$


$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{eff}) \Rightarrow \frac{W}{L} = \frac{g_m}{\mu_n C_{ox} (V_{eff})} = 23.83$$

$$\text{So } R_D = 2.05\text{K}, C_L = 50\text{fF}$$

$$V_{GS} - V_{th} = 0.916\text{V}, W/L = 23.83$$



54)

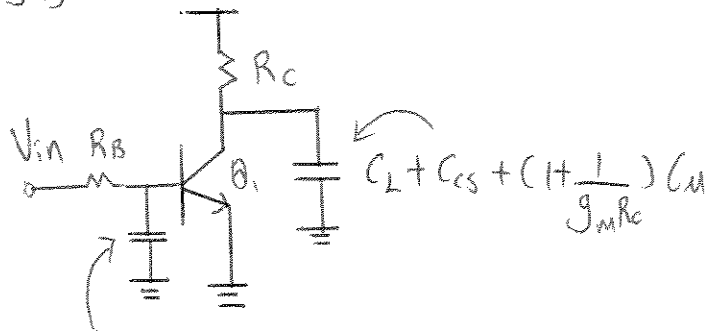

$$C_{\pi} + (1 + g_m R_c) C_{\mu}$$

Low freq Voltage gain: 
$$\frac{V_{out}}{V_{in}} = \frac{-R_c}{1/g_m + \frac{R_B}{\beta + 1}}$$

$$\omega_{out} = \frac{1}{R_c [C_L + C_{cs} + (1 + \frac{1}{g_m R_c}) C_{\mu}]} = (2\pi)(2 \text{ GHz})$$

$$g_m = \frac{I_c}{V_T} = 0.0386 \frac{1}{\Omega}$$

$$g_m = (2\pi)(2 \text{ GHz}) [g_m R_c [C_L + C_{cs}] + g_m R_c (C_{\mu} + C_{\pi})]$$

$$R_c = \left[ \frac{g_m}{(2\pi)(2 \text{ GHz})} - C_{\mu} \right] / (g_m [C_L + C_{cs} + C_{\mu}])$$

$$R_c = 2269.94 \Omega \approx 2.27 \text{ K}\Omega$$


Again, to maximize low freq gain,  $R_B$  should be as small as possible, so  $R_B / V_T \approx R_B$

$$\omega_{in} \approx \frac{1}{R_B (C_{\pi} + C_{\mu} (1 + g_m R_c))} = (2\pi)(500 \times 10^6), g_m R_c = 87.62$$

$$R_B = 687.35 \Omega$$

So,  $R_c = 2.27 \text{ K}\Omega, R_B = 687.35 \Omega$

56)

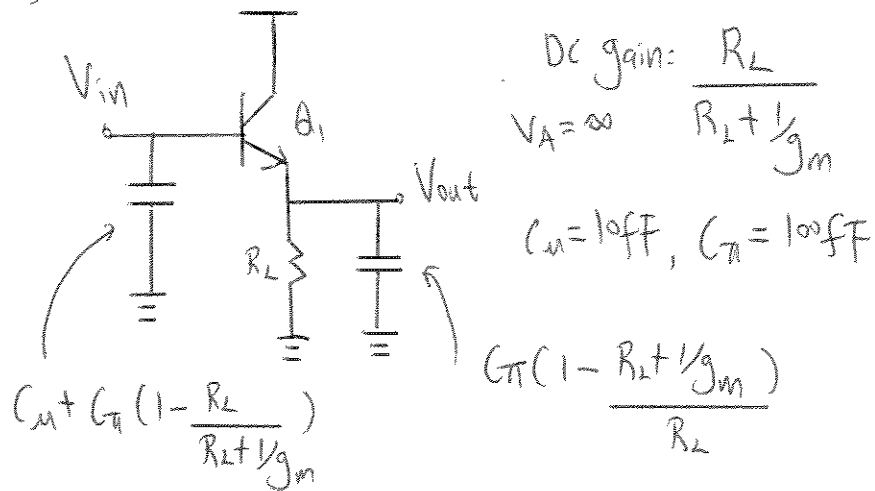

$$C_{in} < 50 \text{ fF} \Rightarrow C_u + C_\pi \left(1 - \frac{R_L}{R_L + 1/g_m}\right) < 50 \text{ fF}$$


$$10 \text{ fF} + 100 \text{ fF} \left(1 - \frac{R_L}{R_L + 1/g_m}\right) < 50 \text{ fF}$$

$$100 \text{ fF} \left(1 - \frac{R_L}{R_L + 1/g_m}\right) < 40 \text{ fF}$$

$$\left(\frac{1/g_m}{R_L + 1/g_m}\right) < 0.4$$

$$R_L > \frac{3}{2g_m} = 38.85 \Omega$$

58)

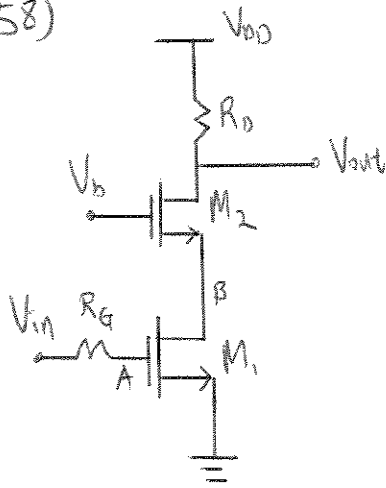

$$\omega_{pin} = 5 \text{ GHz}, \omega_{pout} = 10 \text{ GHz}$$

$$V_{eff} = 200 \text{ mV} (V_{GS} - V_{th}), I_D = 0.5 \text{ mA}$$

$$\lambda = 0, C_{GS} = (2/3) W L C_{ox}$$

$$L = 0.18 \mu\text{m}, \mu_n C_{ox} = 100 \mu\text{A/V}^2$$

$$C_{GD} = W C_o, C_o = 0.2 \text{ fF}/\mu\text{m}$$

$$C_{ox} = 12 \text{ fF}/\mu\text{m}^2$$

$$\text{DC gain from A to B: } -\frac{g_{m1}}{g_{m2}} = 1$$

$$C_{in} = C_{GS} + C_{GD} (1 + g_{m1}/g_{m2}) = C_{GS} + 2 C_{GD}$$

$$I_D = \frac{1}{2} \frac{W}{L} \mu_n C_{ox} (V_{eff})^2 = 0.5 \text{ mA} \Rightarrow \frac{W}{L} = 250$$

$$L = 0.18 \mu\text{m}, W = 45 \mu\text{m}$$

$$\omega_{pin} = (2\pi)(5 \times 10^9) = \frac{1}{R_D \left[ \frac{2}{3} (45)(0.18)(12 \text{ fF}/\mu\text{m}^2) + (0.2)(45)(2) \right]}$$

$$R_D = 384.43 \Omega$$

$$\omega_{pout} = \frac{1}{R_D [0.2 W]} = (10 \times 10^9)(2\pi), W = 45 \mu\text{m}$$

$$\Rightarrow R_D = 1.8 \text{ k}\Omega \quad (1768.4 \Omega \text{ exact value})$$

$$\text{Gain} = |g_m R_D| = \frac{2 I_D R_D}{V_{eff}} = 8.842$$